


Q8 $(\bar{A} + B + \bar{C}) \cdot (A + \bar{C})$

$$(\bar{A} + B + \bar{C}) \cdot (A + \bar{C}) + 0$$

$$(\bar{A} + B + \bar{C}) \cdot (A + \bar{C}) + (B \cdot \bar{B})$$

$$(\bar{A} + B + \bar{C}) \cdot (A + \bar{C} + B) \cdot (A + \bar{C} + \bar{B})$$

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

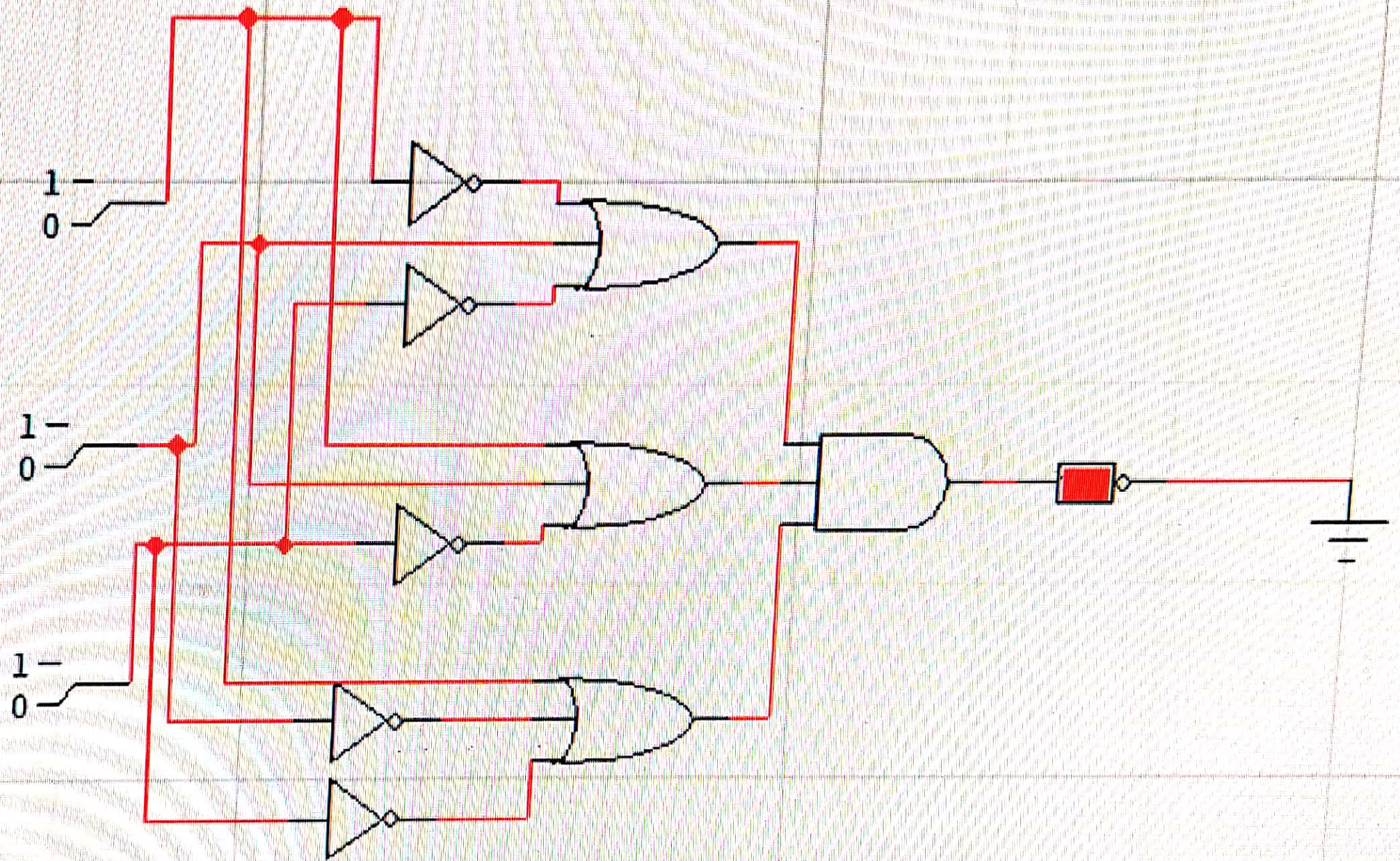

Q4a

	BC				
	00	01	11	10	
A	0	1	0	0	1
B	1	0	1	1	1

$$\underline{b} = \underline{A}C + \bar{A}\bar{C} + B\bar{C}$$

<u>C</u>	IC Type	Required No. of Gates	Gates Per IC	Required No. of ICs
	AND (08)	3	4	1
	OR (32)	2	4	1
	NOT (04)	3	6	1
Total No. of ICs				3