


Digital Logic Design

Muhammad Hassan Khalid

211-5692

① $S = \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D}$

		1			10
1			1		11
		1			01
					00
10	11	01	00		CD
					AB

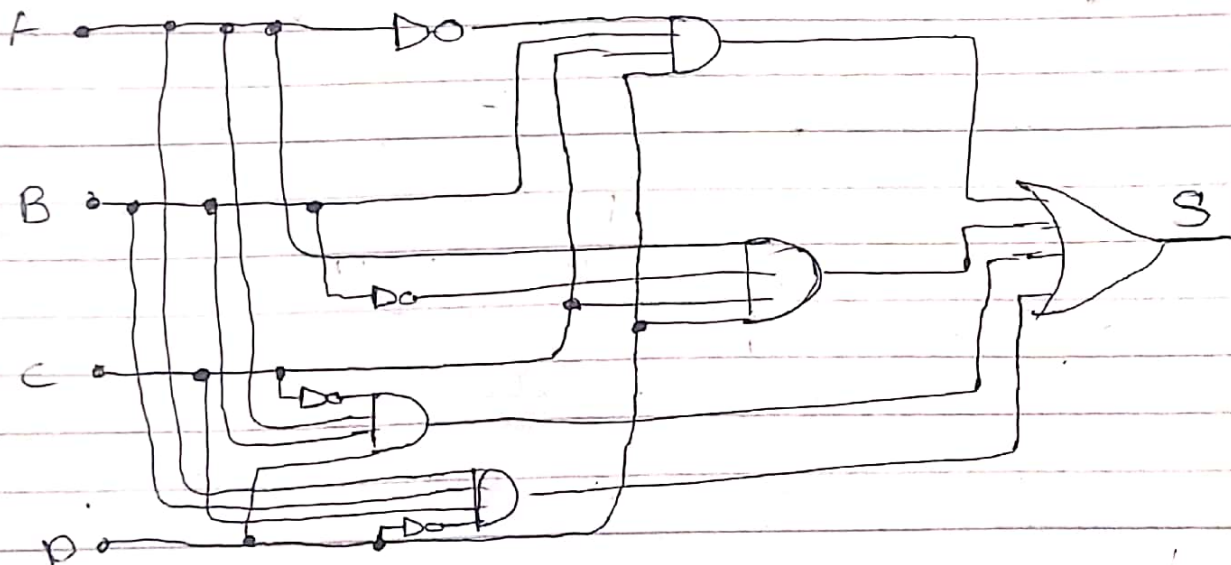


② $S = M \cdot (\bar{L} + P)$

∴ Key

Master Switch = M

Light Beam = L

Pressure Pad = P

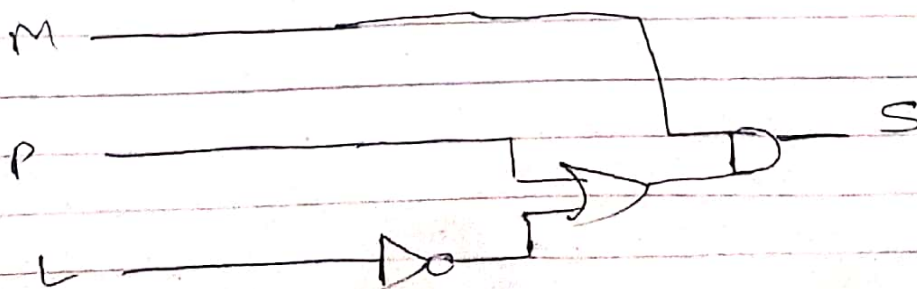


$$S = (A \cdot B) \cdot \bar{C}$$

∴ Key

Bolt A = A
Bolt B = B
Sensor C = C


④

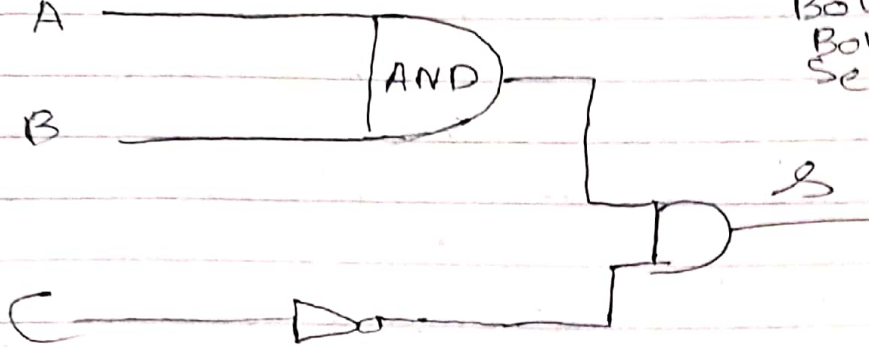

$$S = (A + ((B \cdot R) \cdot \bar{A}) + A \cdot B)$$

∴ Key

Amina = A
Bilal = B
Rahim = R

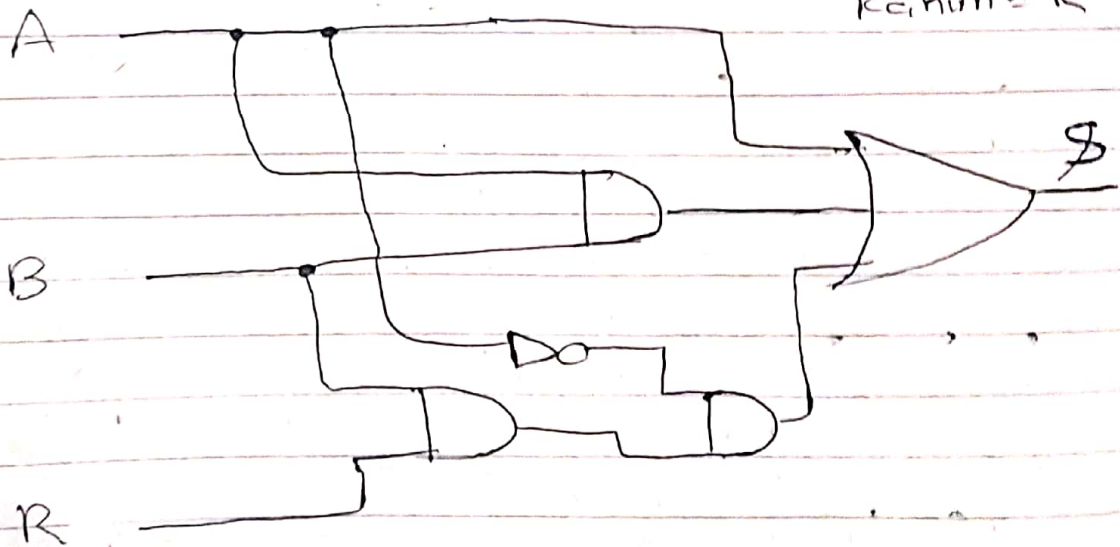

==